

In order that the currents on the $\lambda/2$ dipoles be in phase quadrature, the dipoles may be connected to separate nonresonant lines of unequal length. Suppose, for example, that the terminal impedance of each dipole in a single-bay turnstile antenna is $70 + j0 \Omega$. Then by connecting $70\text{-}\Omega$ lines (dual coaxial type), as in the schematic diagram of Fig. 16-16a, with the length of one line 90 electrical degrees longer than the other, the dipoles will be driven with currents of equal magnitude and in phase quadrature. By connecting a $35\text{-}\Omega$ line between the junction point P of the two $70\text{-}\Omega$ lines and the transmitter, the entire transmission-line system is matched.

Another method of obtaining quadrature currents is by introducing reactance in series with one of the dipoles.¹ Suppose, for example, that the length and diameter of the dipoles in Fig. 16-16b result in a terminal impedance of $70 - j70 \Omega$. By introducing a series reactance (inductive) of $+j70 \Omega$ at each ter-

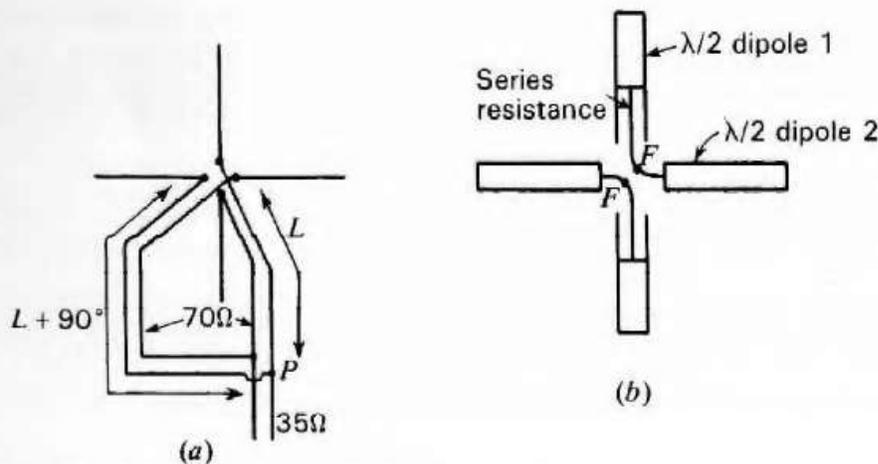


Figure 16-16 Arrangements for feeding turnstile antennas.

¹ G. H. Brown and J. Epstein, "A Pretuned Turnstile Antenna," *Electronics*, **18**, 102-107, June 1945.

minal of dipole 1 as in Fig. 16-16b, the terminal impedance of this dipole becomes $70 + j70 \Omega$. With the 2 dipoles connected in parallel, the currents are

$$I_1 = \frac{V}{70 + j70}$$

and

$$I_2 = \frac{V}{70 - j70} \quad (6)$$

where V = impressed emf

I_1 = current at terminals of dipole 1

I_2 = current at terminals of dipole 2

Thus,

$$I_1 = \frac{V}{99} \angle -45^\circ$$

and

$$I_2 = \frac{V}{99} \angle +45^\circ \quad (7)$$

so that I_1 and I_2 are equal in magnitude but I_2 leads I_1 by 90° . The 2 impedances in parallel yield

$$Z = \frac{1}{Y} = \frac{1}{[1/(70 + j70)] + [1/(70 - j70)]} = 70 + j0 \quad (\Omega) \quad (8)$$

so that a $70\text{-}\Omega$ (dual coaxial) line will be properly matched when connected to the terminals FF .